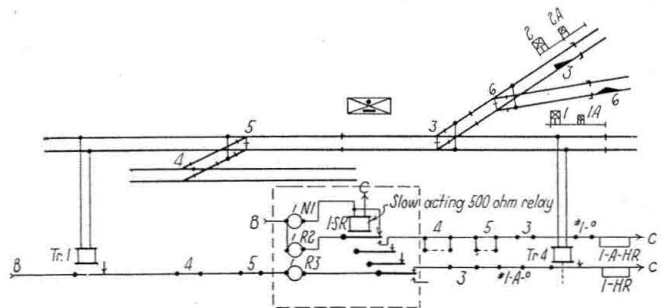




cuit, of course, can be used for signals 2 and 2A and it is also possible that all four of these signals could be operated from one lever by properly selecting the home relay circuit over switches 2 and 3. It should be noted that relay 1-SR, as shown, is a slow-acting 500-ohm relay and the circuit works in the following manner:

Number 1 lever normal picks up relay 1-SR. Pulling



Slow acting stick relay circuit which will select between top and bottom arms by time delay in reversing signal lever

lever 1 quickly, will cause contact 1-R2 to make, causing relay 1-SR to stick over its own point and will also close contact 1-R3 picking up relay 1-HR, thereby clearing high-speed signal 1. If the slow-speed indication is desired, regardless of whether track is clear or not, lever 1 must be pulled slowly from the normal to the reverse position, giving slow-acting relay 1-SR time to open before closing contact 1-R2. This will let relay 1-SR open, which will pick up relay 1A-HR, giving the slow-speed indication of signal 1A.

Huntington, W. Va.


W. H. MILLER,

Signal Cabin Inspector, Chesapeake & Ohio.

(Objectionable feature is that lever must be operated quickly for top arm and very slowly for call-on arm; otherwise takes care of all features required in question.—EDITOR.)
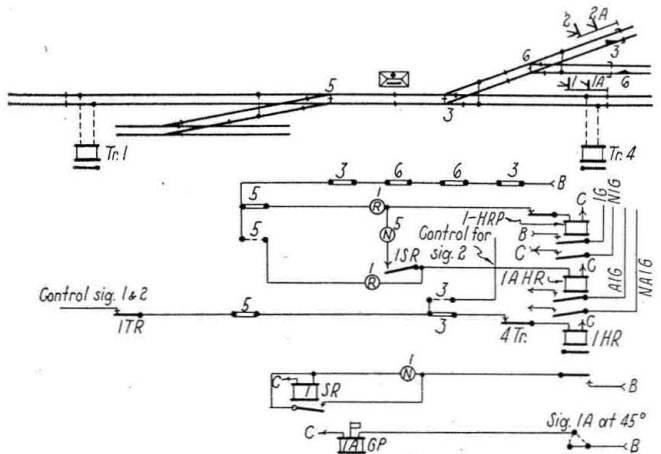
#### Stick Relay Control of Both Top and Bottom Arms Proposed—Signal 1A Cannot Clear Until Lever is Returned to Normal and Then Reversed

THE circuits shown in answer to question 4 are controlled through switch boxes instead of repeater relays, as used on some roads. Signal 4 is controlled by 1HR and 1HRP. Relay 1HR does not break through the lever but is controlled through the track relay to



Circuit arrangement for stick relay control of signals 1 and 1A

the next signal ahead. It is not necessary to take it through switches 3 and 5 but this is an extra check. Signal 1A is controlled by 1SR and 1AHR. Stick re-

lay 1SR will not pick up unless the track relay is open (causing 1HR to drop) and lever 1 is normal. If 1HR is open and lever 1 is normal 1SR will pick up and remain picked up through its front contact after lever 1 is reversed..

If the route is normal and lever 1 is reversed signal 1 will clear because 1SR will be open. When a train enters and shunts 4TR, relays 1HR and 1HRP will drop, but 1AHR will not pick up to clear signal 1A because 1SR will be open. It would be necessary to put lever 1 back to normal and reverse it again to clear signal 1A.

With this arrangement it is impossible for signal 1A to clear for a straight line movement when the track relay is picked up. Furthermore, it will not clear behind a train until the lever is put back normal and then reversed. It will always clear for a diverging route or when the track circuit is out. It is not really necessary to have 5(N) contact in the circuit but it is an extra check to cut the current off of the 1HRP wire when switch 5 is reversed.

The circuits for signals 2 and 2A would be similar. The signal repeater for calling-on arm is shown.

Richmond, Va.

A. G. WALKER,

Circuit Draftsman, Chesapeake & Ohio.


(Only objection is lower-arm is not a call-on, in the sense that a call-on arm can be used for any route at any time it is desired.—EDITOR.)

### What's Wrong Here?

(Can you locate the weakness in any of the following replies to question No. 4, page 152 of the April issue? These were received as answers to the question but for one or more reasons were not considered as practical solutions to the problem.—EDITOR.)
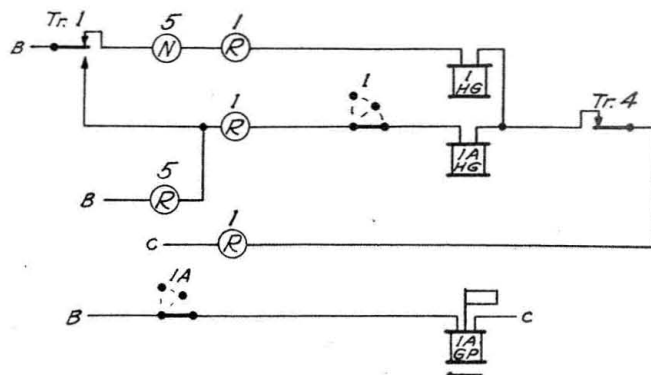
#### Non-Stick Control for Call-On Signal 1A Selected Through Track Relays TR1 and TR4

IN the following solution I have assumed from the track circuit layout that signal 1 may be cleared if track sections TR1 and TR4 are unoccupied. The circuit will function as follows: Should the operator reverse lever 1 with track sections TR1 and TR4 unoc-



Simplified circuit for controlling signals 1 and 1A

cupied, signal 1 will clear. The circuit for signal 1A is open and there is no possibility of a "bob" on the signal. When the train passes the signal, relay TR4 will de-energize, opening the circuit for signal 1, causing it to return to the stop position. As the rear of the train clears section TR4 the control circuit for signal 1A is completed through the back contact of TR1 and the front contact of TR4, causing signal 1A to clear automatically. When the train clears section TR1 the circuit for signal 1A is opened and that for signal 1 is


closed, causing signal 1 to clear and 1A to return to the horizontal position.

Control of signals 2 and 2A can be effected in the same manner, using the track relay at the signal location (not designated in original signal plan) and relay TR<sub>1</sub>.

CIRCUIT ENGINEER.
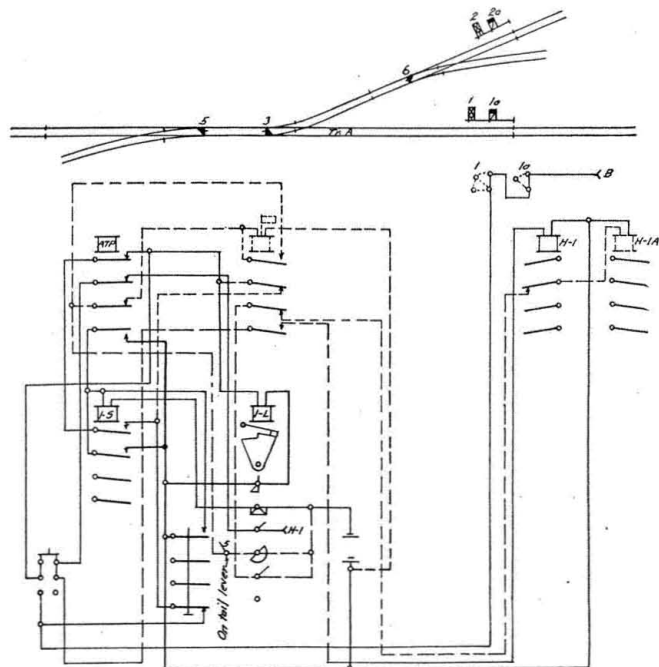
### Standard Circuit Scheme Modified Slightly to Obtain Desired Operation of Call-On Signals

THE drawing shows in dotted lines what will be necessary to add to a standard circuit to control a call-on signal without a push button or other mechanical device. Indicator on indicating relay will show clear when switch 5 is normal, track relay energized and sig-



Modified circuit plan to obtain operation of call-on arms 1A and 2A


nal lever reversed. The indicator on indicating relay will show stop when signal lever is reversed and either switch 5 reversed or the track relay de-energized.

CIRCUIT DRAFTSMAN,
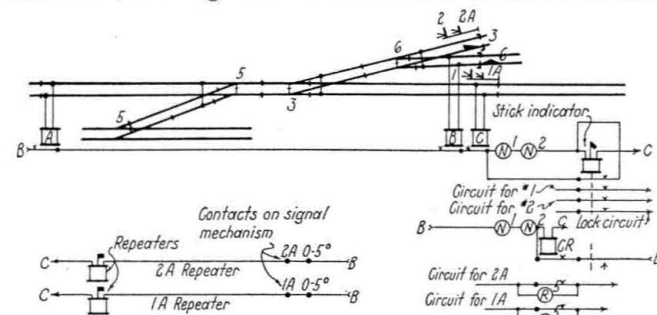
### Circuit Scheme Employs One Stick Relay and an Additional Track Circuit

IN the following circuit arrangement in answer to question 4 in the April issue, I have not shown any wiring for signals 1, 1A, 2 or 2A as they can be wired to suit the practice of any individual road. The top signals, 1 or 2, must be controlled through a stick indicator. For simplicity, however, I have shown only one stick indicator circuit to control both high signals. This is possible because the position of switch 3 determines which of these signals should be cleared, on account of the mechanical locking of the machine. Inspection of the circuit showing the control of stick relay CR will show that after a train passes signal 1 or 2 (according to the lineup) and the signal has returned to the stop position closing the lock circuit, returning the signal lever normal, will pick up stick relay CR, after which this relay will be held up by the back point of the stick indicator. As the control circuits for signals 1A and 2A are broken through the front points of the stick relay CR, either of these signals can be cleared only when desired by the

operator through reversal of the corresponding signal lever. Repeater circuits are shown for signals 1A and 2A. Although the stick indicator is shown as tak-



Suggested circuit scheme for accomplishing desired operation of call-on signals


ing battery at track relay A, this can be extended as the stick indicator should control as far as the signal ahead.

Owing to the fact that signals 1A and 2A control the route over switch 5 reversed, the contact on stick relay CR controlling signals 1A and 2A, must be shunted by a multiple jumper when switch 5 is reversed.

GENERAL SIGNAL FOREMAN.
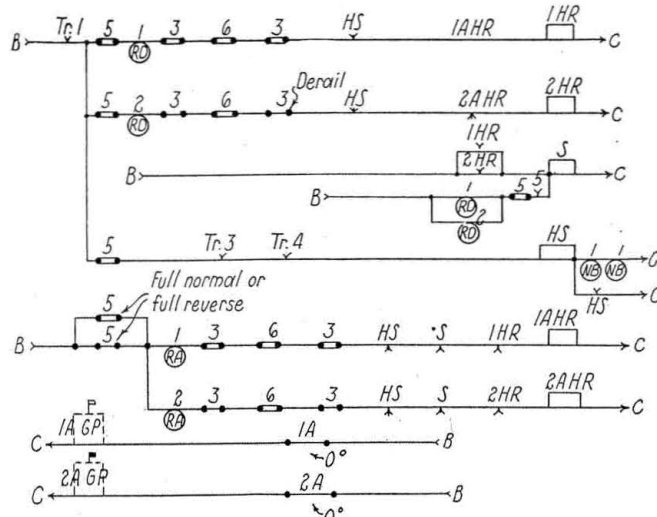
### Control Scheme Utilizes Additional Short Track Section

IN this solution to question No. 4 in the April issue I have added TR<sub>3</sub> in the short track section extending from a point midway between switch 3 and switch 6, and signals 2 and 2A. The signal to be cleared is selected through a front or back contact on a stick relay (HS) which is picked up through front contacts on the track relays in the block but which is open when switch 5, leading to the dead tracks, is re-



Written circuit for call-on signal control

versed. With this scheme it is impossible to use the call-on signal when the block is clear. An additional stick relay S is provided to prevent the call-on signal from clearing immediately after a train passes through the interlocking limits. In this circuit relay S picks up over a front contact on either of the high signal home relays and is held up until the signal is restored to normal. The pick-up circuit of this relay is through a circuit controller on switch 5 and this enables a follow-up move to be made through switch 5 reversed before the first train clears the interlocking limits, by opening the stick relay circuit S and allowing the call-on signal 1A to clear.

E. W. R.