



# What's the Answer?

An open forum for the discussion of maintenance and construction problems encountered in the signaling field. *Railway Signaling* solicits the co-operation of its readers both in submitting and answering any questions of interest.

TO BE ANSWERED IN A SUBSEQUENT ISSUE

- (1) *What type of construction do you prefer for insulating tie plates for interlocked switches?*
- (2) *Do you use switch indicators in automatic block signal territory? Have you abandoned the use of switch indicators?*
- (3) *What tests are made on your road to be sure that automatic highway crossing signals are operating as intended; who makes the tests; how often, and what records are made?*
- (4) *Do you use a 2-ohm track relay or a 4-ohm? If you use both how do you select the one best fitted to meet any particular track circuit conditions?*
- (5) *At an automatic crossing protection layout without switches or derails, what provision should be made for release of signaling in event of trouble?*


## Several Effective Trap Circuit Schemes

*"Can you locate the defect in the trap circuit in the sketch below? Can a simpler and better circuit be designed?"*

\* \* \*
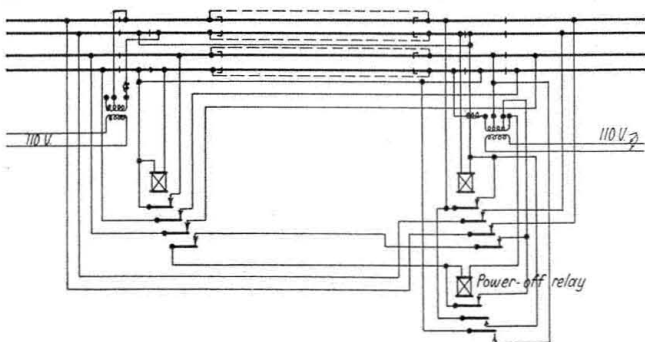
### QUESTION NO. 1—CAN YOU REMEDY THIS TRAP CIRCUIT DEFECT?

I am submitting herewith a trap circuit that has a weak point, which your readers perhaps would be interested in pointing out and correcting. If anything happened to the power-off relay to make it stay down it might remain so undetected for some time, and would result in false clear signals, since it would cut out the protection for the insulated central span. That is, with



Trap circuit for a-c. track circuit operation which employs a power-off relay


the power-off relay open, the "trap" would be ineffective.

—D. G.

\* \* \*
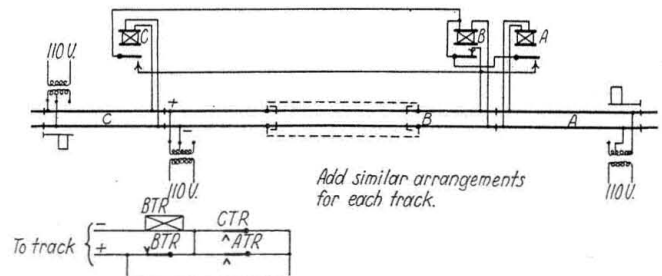
### Proposed Circuit in July Issue of *Railway Signaling* Would Not be Feasible Because Power Failure Would Make Signals Inoperative

THE accompanying trap circuit sketch will, I believe, answer the second part of the question. Since both written and detailed wiring circuits are submitted in my proposed circuit, it would seem that a descriptive explanation is hardly necessary. As to trap cir-



Trap circuit scheme which will better answer the purpose than the one submitted in the July issue

cuits in general, there are many different designs, but I think the one furnished will answer satisfactorily. It can be used on either single or double track with train operating in both directions and if, for any reason, the stick track relay should fail to pick up, the signals will always


show the most restrictive position and the chances for the relay failing to shunt is not any greater than with any other track relay.

As to the weak point in the trap circuit, published in the July issue, I do not think I understand fully what is called "the power-off relay" because the way I understand the circuit, the "power-off relay" will never drop on account of being "stuck" up on one side direct to the negative side of the transformer and on the other through its own point direct to the positive side of the transformer. Only an interruption in the a-c. line would drop this relay. If this is the intention, all track relays would also fail with an interruption in the a-c. line and the signal system as a whole would become inoperative.

Nashville, Tenn. E. W. ANDERSON,  
Signal Designer, Nashville, Chattanooga & St. Louis.

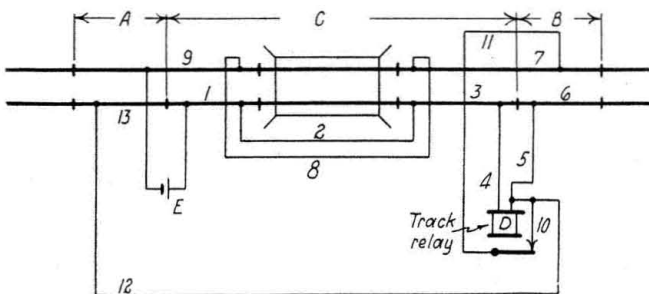**This Trap Circuit Scheme Employs but One Track Relay**

IF anything happened to the power-off relay in the circuit published in the July issue causing the relay to remain de-energized, current flowing to the track relays would result in false-clear signals. I believe the trap circuit shown in the sketch herewith is workable and simple. Any trap circuit to be effective must operate in both directions and this requirement is fulfilled by the simple scheme suggested. It will be noted that my circuit employs a normally energized stick relay. The single rail sections *A* and *B* are release and pick-up sections for the stick relay *D*, the particular func-



Simplified trap circuit which employs but one trap relay and one line wire

tion of these sections depending upon the direction of train movement. These short track sections may be from 15 to 33 ft. in length.




A train will, upon passing section *A* and entering section *C*, shunt the track relay *D* and the latter will not pick up again until the train has reached the pick-up section *B*. The pick-up circuit is completed by the current flow from track battery *E*, track connection 4, coils of stick relay *D*, track connection 5, rail 6, wheels and axles of train, rail 7, jumper 8, rail 9 and back to battery. This relay when once picked up will remain picked up through the former circuit in conjunction with jumper wire 10 from the front point of the relay and track connection 11. Conversely a train movement in the opposite direction will de-energize and pick up the stick relay *D*. For a reverse movement, wire 12, which is connected to the rail in section *A* is used for pick-up purposes.

The outstanding feature of this circuit is its simplicity as it requires only one line wire and one track relay. It can of course be operated on either d-c. or a-c. and can be used for either single-track or double-track installations.

Chariton, Iowa. T. A. HOUSE,  
Signal Maintainer, Chicago, Burlington & Quincy.

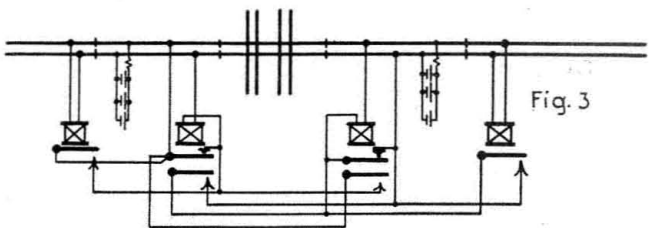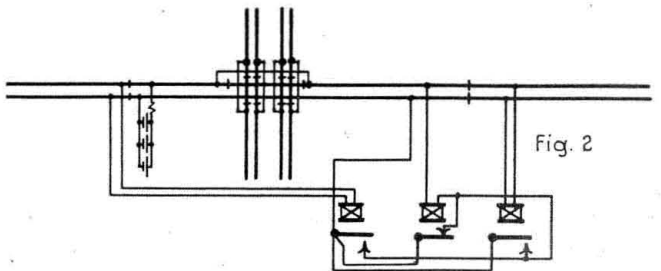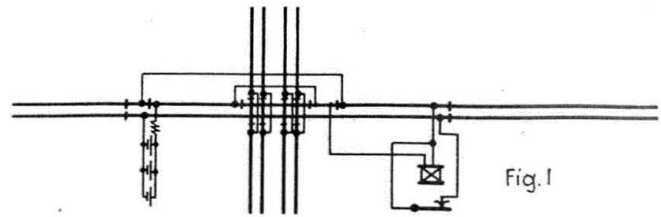**Three Different Schemes Suggested for Varying Degrees of Trap Circuit Protection**

INASMUCH as I have not had much experience with the operation of alternating current track circuits I do not believe that I care to discuss the circuit submitted in the July issue. I am, however, enclosing three sketches of trap circuits that are used by the Delaware & Hudson. The first scheme is used wher-



Three trap circuits for various degrees of protection

ever we are not very particular about securing the maximum amount of trap circuit protection. Where the maximum amount of protection is required it is our practice to use the circuit shown in scheme 2. Where it is not desired to bond around the crossing or dead section of track, the circuit shown in scheme 3 is employed. The latter circuit also affords maximum protection.

Albany, N. Y. A. VALLEE,  
Supervisor of Signal Construction, Delaware & Hudson.

**If the Power-Off Relay Should Remain Open There Would Be a False Clear Failure If the Insulated Trap Section Was Occupied**

IN the trap circuit published in the July issue, the power-off relay serves but one purpose and that is to pick up the track relays over the back contacts of the power-off relay when the alternating current power "come on" after an outage. Apparently without some such an arrangement the track relays would fail to pick up until the train passed over the track circuit. However, the trouble with the circuit is due to the fact that if the power-off relay should remain open due to an open-circuited coil, broken wire, or some other cause, there would be a false clear failure if the insulated section was occupied.

The sketch submitted herewith I believe takes care of these features and at the same time eliminates the possibility of a false clear failure. It will be noted that I have shown a power-off relay in series with the

